






#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
7.	R1_S2	Vishay-Dale	CRCW1206430KJNEA Series= CRCW..e3	Res= 430.0 kOhm Power= 250.0 mW Tolerance= 5.0%	1	\$0.01	 1206 11 mm ²
8.	R2_S1	Vishay-Dale	CRCW0402150RJNED Series= CRCW..e3	Res= 150.0 Ohm Power= 63.0 mW Tolerance= 5.0%	1	\$0.01	 0402 3 mm ²
9.	R2_S2	Panasonic	ERJ-6GEYJ474V Series= ERJ-6GE	Res= 470.0 kOhm Power= 125.0 mW Tolerance= 5.0%	1	\$0.01	 0805 7 mm ²
10.	R3_S1	Panasonic	ERJ-6GEYJ242V Series= ERJ-6GE	Res= 2.4 kOhm Power= 125.0 mW Tolerance= 5.0%	1	\$0.01	 0805 7 mm ²
11.	R3_S2	Vishay-Dale	CRCW1206560KJNEA Series= CRCW..e3	Res= 560.0 kOhm Power= 250.0 mW Tolerance= 5.0%	1	\$0.01	 1206 11 mm ²

Design Inputs


#	Name	Value	Description
1.	FilterType	Lowpass	
2.	FilterResponse	Bessel	
3.	FilterOrder	3.0	
4.	FilterTopology	Multiple_Feedback	
5.	NumberOfStages	0.0	
6.	PassbandFrequency	100.0 m	
7.	StopbandAttenuation	-45.0	
8.	StopbandFrequency	5.0 k	
9.	Gain	1.122	
10.	DualSupply	+/-5.00 V	Power supply(s) to active chips
11.	ResistorTolerance	E24	Resistor series - 5% Passive resistor tolerance
12.	CapacitorTolerance	E12	Capacitor series - 10% Passive capacitance tolerance
13.	SeedCapacitance	1.0 μ	Seed Capacitance to start design of filter

Design Assistance





1. **LM741CN/NOPB** Product Folder : <http://www.ti.com//product/LM741> : contains the data sheet and other resources.

Filter Stage :1

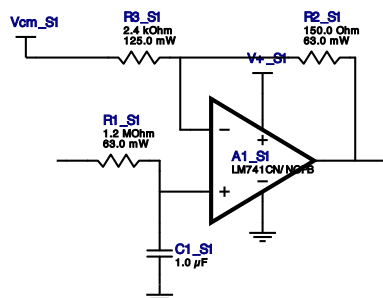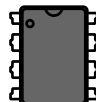Cutoff Frequency 132.7 mHz
 Min GBW Reqd 7.028 Hz
 Stage Gain 1.059 V/V
 Stage Q 500.0 m
 Stage Topology Multiple_Feedback




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments, Inc.	LM741CN/NOPB	GbwTyp= 1.0MHz VccMin= 10.0 V VccMax= 36.0 V	1	\$0.22	 P0008A 116 mm ²
2.	C1_S1	CUSTOM	CUSTOM Series= ?	Cap= 1.0 uF VDC= 0.0 V Tolerance= 0.0 %	1	NA	CUSTOM 0 mm ²
3.	R1_S1	Vishay-Dale	CRCW04021M20JNED Series= CRCW...e3	Res= 1.2 MOhm Power= 63.0 mW Tolerance= 5.0%	1	\$0.01	 0402 3 mm ²
4.	R2_S1	Vishay-Dale	CRCW0402150RJNED Series= CRCW...e3	Res= 150.0 Ohm Power= 63.0 mW Tolerance= 5.0%	1	\$0.01	 0402 3 mm ²
5.	R3_S1	Panasonic	ERJ-6GEYJ242V Series= ERJ-6GE	Res= 2.4 kOhm Power= 125.0 mW Tolerance= 5.0%	1	\$0.01	 0805 7 mm ²


Filter Stage :2

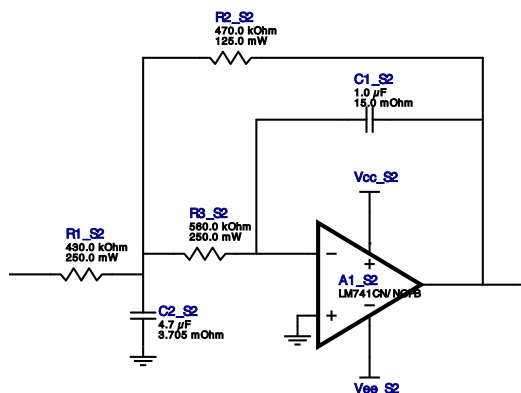Cutoff Frequency 145.238 mHz
 Min GBW Req'd 10.631 Hz
 Stage Gain 1.059 V/V
 Stage Q 691.015 m
 Stage Topology Multiple_Feedback



Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S2	Texas Instruments, Inc.	LM741CN/NOPB	GbwTyp= 1.0MHz VccMin= 10.0 V VccMax= 36.0 V	1	\$0.22	 P0008A 116 mm ²
2.	C1_S2	Kemet	C0805C105K4RACTU Series= X7R	Cap= 1.0 uF ESR= 15.0 mOhm VDC= 16.0 V Tolerance= 10.0 %	1	\$0.02	 0805 7 mm ²
3.	C2_S2	MuRata	GRM31CR71C475KA01L Series= X7R	Cap= 4.7 uF ESR= 3.705 mOhm VDC= 16.0 V Tolerance= 10.0 %	1	\$0.10	 1206_190 11 mm ²
4.	R1_S2	Vishay-Dale	CRCW1206430KJNEA Series= CRCW..e3	Res= 430.0 kOhm Power= 250.0 mW Tolerance= 5.0%	1	\$0.01	 1206 11 mm ²
5.	R2_S2	Panasonic	ERJ-6GEYJ474V Series= ERJ-6GE	Res= 470.0 kOhm Power= 125.0 mW Tolerance= 5.0%	1	\$0.01	 0805 7 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
6.	R3_S2	Vishay-Dale	CRCW1206560KJNEA Series= CRCW..e3	Res= 560.0 kOhm Power= 250.0 mW Tolerance= 5.0%	1	\$0.01	 1206 11 mm ²

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.